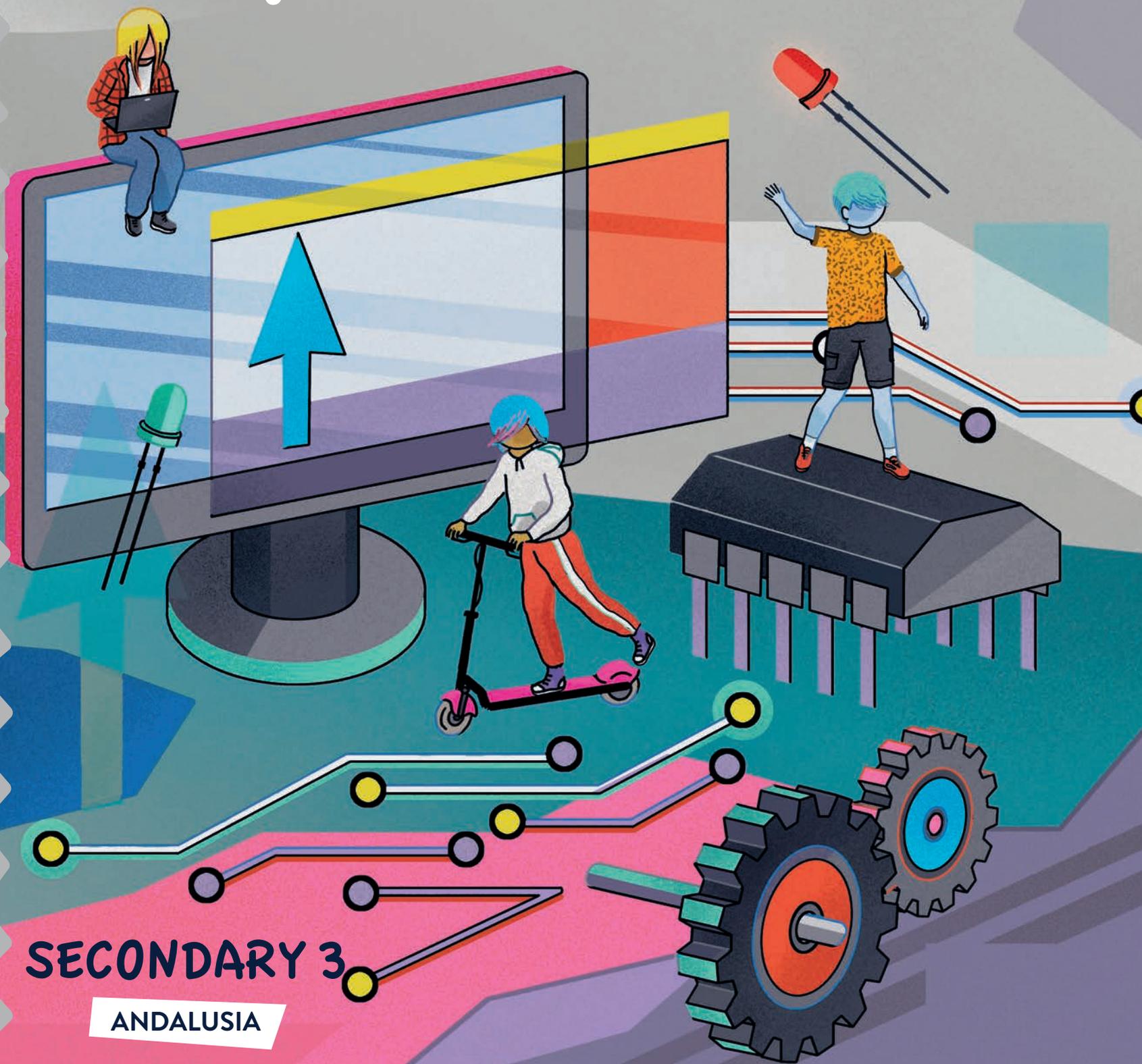




CORE

TECHNOLOGY



SECONDARY 3

ANDALUSIA

1 An electrical circuit

An electric circuit is a path for the flow of negatively-charged particles called **electrons**. These particles can flow as electric **current**¹.

Electric current is a continuous flow of electrons through a circuit.

Parts of an electric circuit

An electric circuit consists of various **components**: generators, conductors, switching devices and loads.

Generators provide electric current and **conductors** carry it through the circuit. **Switching devices**² control the flow of electricity, while **loads** transform it into other types of energy, such as light, heat or motion.

Circuit diagrams


We use standard symbols in diagrams of electrical and electronic circuits. This makes the diagrams easier to understand at a **glance**³.



¹**current**: continuous, flowing movement.

²**device**: tool or machine that perform an action.


³**glance**: a quick look.

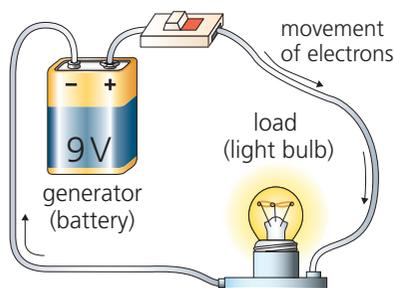

Generators			
Electrochemical cell		Battery	
Loads			
Light bulb	Resistor	Motor	Bell
Switching devices			
Switch	Push button	Three-way switch	Relay
Safety elements			
Fuse			

CLIL activities

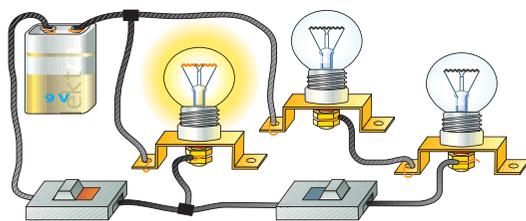- 1 In your notebook, draw a diagram of the circuit using standard symbols.



- 2 Listen to the four sentences. Write *true* or *false*. Correct the false sentences.

- 3 Work in pairs. Discuss the differences between the following components of a circuit.

- a. a battery and a relay
- a. a wire and a light bulb
- a. a bell and a fuse

A ... can/uses/is for ... but/while/unlike a ... which can/uses/is for ...

- 4 List electrical devices in your home. Explain if they are easy and safe to use to a classmate.

A ... is/isn't very safe because ...

5 Electronics

Electronic symbols	
Resistor	
Capacitor	
Diode	
LED	

Electronics involves the study of circuits and components that modify the intensity, direction and properties of electric currents.

Electronic components

Fixed resistances or resistors

A fixed resistance (or **resistor**) opposes the flow of electric current. Its value in ohms (Ω) is shown by a code of coloured stripes. The first two stripes give us a two-digit number. The third stripe tells us how many zeroes to add. The fourth stripe gives the tolerance, which is the maximum deviation from the labelled value.

	gold	black	brown	red	orange	yellow	green	blue	purple	grey	white
number			1	2	3	4	5	6	7	8	9
multiplier	$\times 0.1$	$\times 1$	$\times 10$	$\times 10^2$	$\times 10^3$	$\times 10^4$	$\times 10^5$	$\times 10^6$	$\times 10^7$	$\times 10^8$	$\times 10^9$
tolerance	$\pm 5\%$										

Variable resistances or potentiometers

The value of a variable resistance (or **potentiometer**) can be adjusted between zero and the maximum value specified by the manufacturer.

Resistances affected by physical factors

- **Thermistors** are affected by **temperature**. There are two types:
 - **PTC** (positive temperature coefficient): the higher the temperature, the more resistance the thermistor offers.
 - **NTC** (negative temperature coefficient): the higher the temperature, the less resistance the thermistor offers.
- **Light dependent resistors** (LDR) can be used as light sensors because they offer less resistance when there is more light.


CLIL activities

- 15 Work in pairs. Use the colour code to find the value of the resistors below. Why do you think they are different sizes?



- 16 How are capacitors similar to batteries? What happens when a capacitor is depleted?

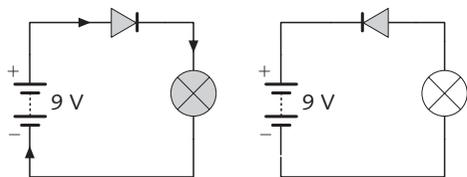- 17 What do the diagrams below show? Which circuit is active?




- 18 Listen to the four students. What mistakes do they make? Correct them in your notebook.

Capacitors	Diodes
A capacitor can store electrical energy and use it to power a device, such as a light bulb. The charge that a capacitor can store is measured in farads (F) .	A diode only allows current to flow in one direction. It has two electrodes: an anode (A) and a cathode (K) . A light emitting diode (LED) produces light when current flows through it.

Transistors

A **transistor** is a switch that is activated by a small electric current. Transistors are made of semiconductor materials and have three electrodes: the base (B), the collector (C) and the emitter (E).


- When no electrons are flowing through the base, electrons cannot flow from C to E. The transistor is in the **cutoff region**.
- When a lot of electrons are flowing through the base, the route from C to E is totally open. The transistor is in the **saturation region**.
- When the flow of electrons through the base is between the cutoff and saturation regions, the transistor is in the **active region**. The flow of electrons from C to E is proportional to the flow of electrons through B.

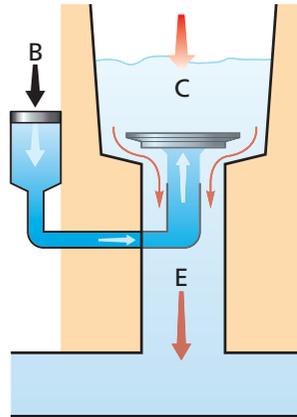

Integrated circuits

Integrated circuits contain a variety of miniature electronic components, such as transistors, resistors and capacitors. For example, a UL-N2803A integrated circuit has eight pairs of Darlington transistors.

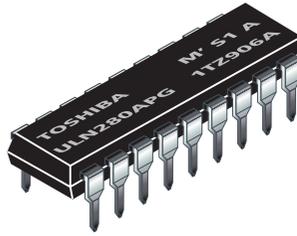Integrated circuits can be **analogue** or **digital**. We can use them to make amplifiers, radio receivers, microprocessors and other devices.



Basic devices with electronic components

We can build various devices with the electronic components discussed in the previous section. Here are two examples:

A timer

The first diagram on the right represents a timer that shuts off automatically.

- At first, there is no current flowing through the base. The transistor is in the cutoff region. When we push the button, current flows through the base, the transistor is activated and the LED turns on. The capacitor also begins to charge.
- When we release the button, the LED stays on for some time, using current from the capacitor. When the capacitor runs out of energy, the transistor cuts off and the LED turns off.

A security alarm

The second diagram on the right represents an alarm that rings when a cable breaks.

- When the cable (AB) is connected, electrons don't flow through the base. The cable is an easier route for the electrons to follow.
- When the cable is broken, electrons flow through the base. When the base is saturated, current flows from the collector to the emitter. This activates the alarm bell.

CLIL activities

19 Listen to the four sentences. In your notebook, write what they describe.

20 What devices in your home have timers that shut off automatically? Why are they necessary?

The ... has a timer. It shuts off because ...

21 **STEAM TASK** Design a circuit for a light that turns on automatically when it gets dark. Use these components: a 4.5 V battery, a light dependent resistor (LDR), an LED and a 2N3055 transistor.

